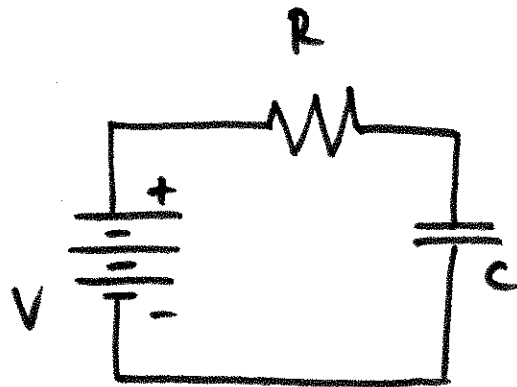




RC circuits - charging & discharging a capacitor

The basic circuit:



components:

 resistor, resistance R (ohms)

 capacitor, capacitance C (farads)

 battery, voltage V (volts)

Essential facts:

(1) $V = V_R + V_C$ (Kirchhoff's voltage law)

V_R = voltage across resistor

V_C = voltage across capacitor

(2) $V_R = IR$, I = current (in amps) (Ohm's Law)

(3) $I = C V_C'$ How capacitors charge/discharge

Putting these essential facts together, we get a 1st-order ODE:

$$V_R + V_C = V \quad (\text{Kirchhoff})$$

$$\Rightarrow IR + V_C = V \quad (\text{Ohm's Law})$$

$$\Rightarrow (CV'_C)R + V_C = V \quad (\text{capacitor behavior})$$

$$\Rightarrow RC V'_C + V_C = V$$

Note: R, C, V are known constants

$V_C = V_C(t)$ = voltage across the capacitor
is the only unknown.

$$\Rightarrow V'_C + \frac{1}{RC} V_C = \frac{1}{RC} V$$

$$\Rightarrow \left\{ \begin{array}{l} V'_C = \frac{1}{RC} (V - V_C) \\ \text{initially, } V_C = V_C(0) = 0 \end{array} \right\} \begin{array}{l} \text{initial-value problem} \\ \text{to be solved} \end{array}$$

$$\begin{cases} V_c' = \frac{1}{RC}(V - V_c) \\ V_c(0) = 0 \end{cases}$$

Solution:

$$\frac{V_c'}{V - V_c} = \frac{1}{RC}$$

$$\Rightarrow \frac{d}{dt} (-\ln(V - V_c)) = \frac{1}{RC}$$

$$\text{integrate} \Rightarrow -\ln(V - V_c) = \frac{t}{RC} + k$$

$$\ln(V - V_c) = -\frac{t}{RC} + k$$

$$\text{exponentiate} \Rightarrow V - V_c = k e^{-t/RC}$$

$$\text{Then solve for } V_c: V_c(t) = V - k e^{-t/RC}$$


$$\text{Since } V_c(0) = 0, k = V.$$

$$\text{Thus, } V_c(t) = V - V e^{-t/RC} = V(1 - e^{-t/RC})$$


for $t \geq 0$!

Plot of $V_c(t) = V(1 - e^{-t/\tau_c})$:


step 1: e^{-t/τ_c}

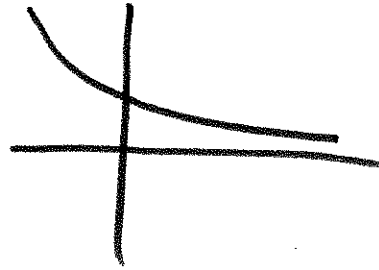


step 2: $-e^{-t/\tau_c}$

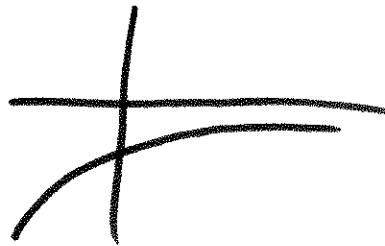

step 3: $1 - e^{-t/\tau_c}$

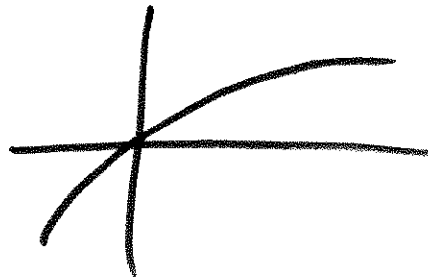


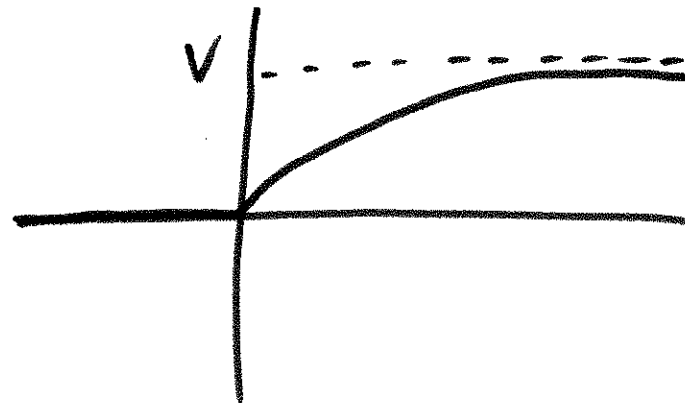step 4: remember that
 $V_c(t) \equiv 0$ for
 $t \leq 0$
and multiply $(1 - e^{-t/\tau_c})$
by V



This is
the voltage
 $V_c(t)$ on the
capacitor as it
charges.

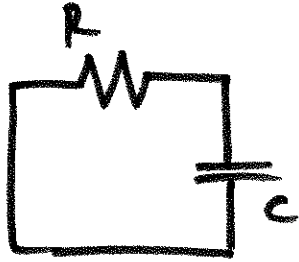Discharging the capacitor: remove the power source



$$\text{Now } V_R + V_C = 0, \quad V_C(0) = V \quad (\text{fully charged})$$

$$\Rightarrow IR + V_C = 0$$

$$\Rightarrow (C V_C') R + V_C = 0$$


$$\Rightarrow RC V_C' + V_C = 0$$

$$\Rightarrow V_C' = -\frac{1}{RC} V_C$$

$$\Rightarrow V_C(t) = k e^{-\frac{t}{RC}}$$

$$\Rightarrow V_C(t) = V e^{-\frac{t}{RC}} \quad \text{since } V_C(0) = V.$$

Discharging:

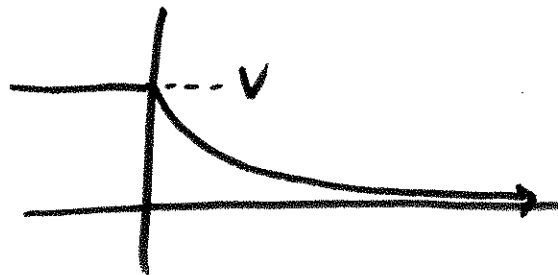

Together:

